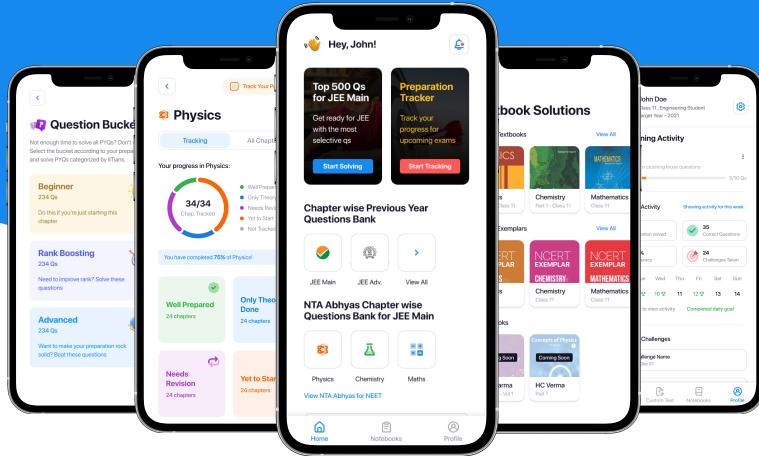




# MARKS



## The only app you need to prepare for



JEE MAIN



JEE ADV.



BITSAT



WBJEE



MHT CET



and more...



4.8

Rating on Google Play

50,000+

Students using daily

2,00,000+

Questions available

### With MARKS app you can do all these things for free 😍

- ✓ Solve Chapter-wise PYQ of JEE Main, JEE Advanced, NEET, BITSAT, WBJEE, MHT CET & more
- ✓ Create Unlimited Custom Tests for any exam
- ✓ Attempt Top Questions for JEE Main which can boost your rank
- ✓ Track your exam preparation with Preparation Trackers
- ✓ Complete daily goals, rank up on the leaderboard & compete with other aspirants



4.8

Rating on Google Play

50,000+

Students using daily

2,00,000+

Questions available



## SEMICONDUCTORS

Semiconductors : Electrical properties of which lie between conductor and insulators.

Semiconductors are materials that have a small energy gap of the order of 1eV. At 0K (absolute zero), the semiconductors behave like insulators.

Intrinsic Semiconductors (pure) : Semiconductor which are free from impurity.

Intrinsic Semiconductors have an equal number of electrons in conduction band and holes in valence band

$$n_e = n_h$$

where  $n_e$  = number of electrons per unit volume

$n_h$  = number of holes per unit volume

$$n_e \times n_h = n_i^2$$

$n_i$  = intrinsic charge carrier density or intrinsic charge carrier concentration

Doped or Extrinsic Semiconductors : Semi conductors doped or added with certain impurity to increase its conductivity.


N-Type : In N type of semiconductor electrons are majority charge carriers and holes are minority charge carriers.

P Type : In P type semiconductors holes are majority charge carriers whereas electrons are minority charge carriers.
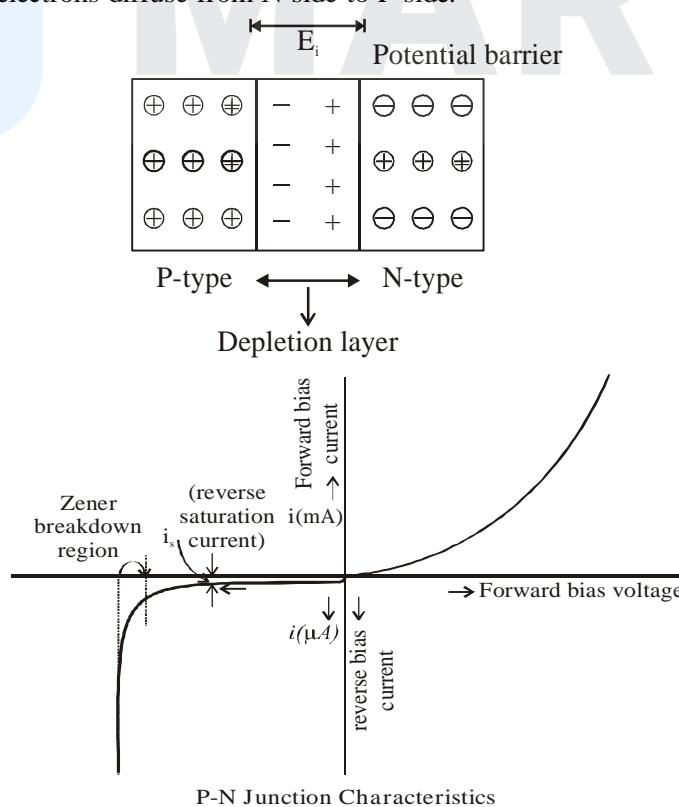
## Semiconductor Devices

The P-N junction Diode :

P side of P-N junction has holes as a majority charge carriers and electrons as a minority charge carriers whereas N side has electrons as a majority charge carriers and holes as a minority charge carriers. holes diffuse from P side to N side whereas electrons diffuse from N side to P side.



### Dynamic Resistance :

$$R = \frac{\Delta V}{\Delta i}$$

Where  $\Delta V$  denotes a small change in the applied potential difference and  $\Delta i$  denotes corresponding small change in current.

Dynamic Resistance is equal to the reciprocal of the slope of the i-V characteristic.


Photodiode : When a light of proper wavelength falls on the junction, new electron-hole pairs are created. The number of charge carriers increases and hence the conductivity of the junction increases. If the junction is connected in some circuit, the current in the circuit is controlled by the intensity of the incident light.

Light-emitting Diode (LED) : When a conduction electron makes a transition to the valence band to fill up a hole in P-N junction, the extra energy is emitted as a photon. If the wavelength of this photon is in the visible range one can see the emitted light. Such a P-N junction is known as light emitting diode (LED).

Zener diode : A diode operated in Zener break down mode is called Zener diode. In this type of mode of operation current increases rapidly but voltage remains almost constant. Thus it is used to obtain constant voltage output.

P-N Junction as a Rectifier : PN Junction can be used to convert A.C into unidirectional current. (DC)

#### (a) Half wave rectifier

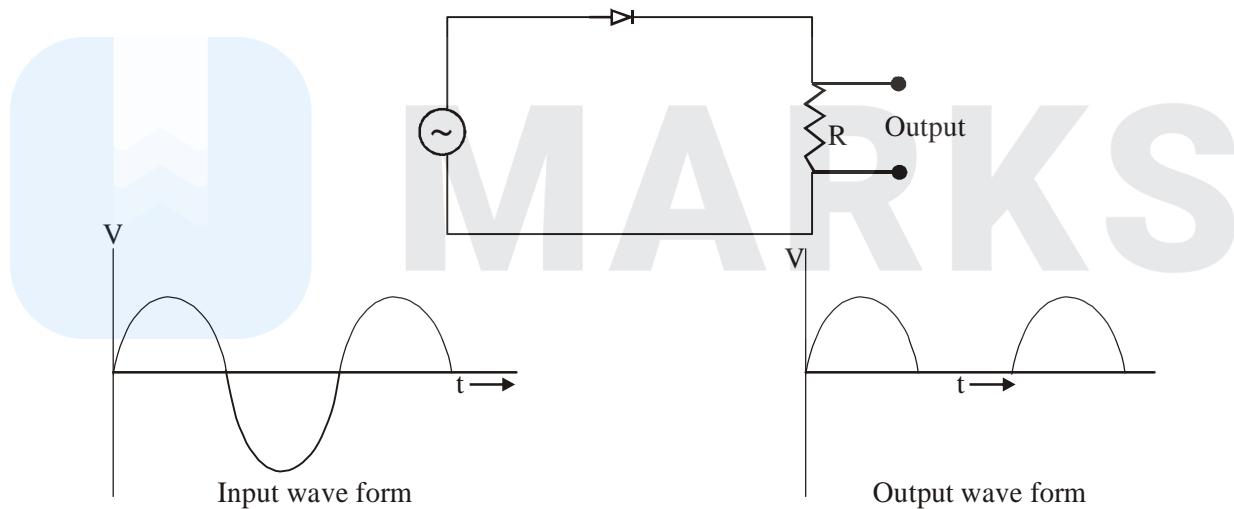


$$\text{Average out put current} = \frac{I_o}{\pi}$$

where  $I_o$  = amplitude of the input current

$$\text{R.M.S. Value of output current} = \frac{I_o}{2}$$

## (b) Full Wave rectifier


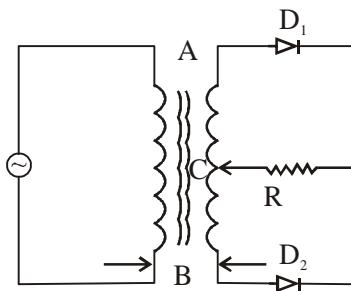


If  $V_A > V_C > V_B$

If  $V_B > V_C > V_A$

$D_1$  Conducts

$D_2$  Conducts

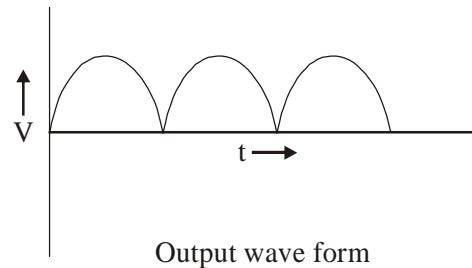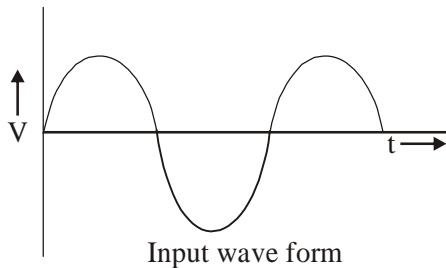

$$\text{Average output current} = \frac{2I_o}{\pi}$$

$$\text{R.M.S. Value of output current} = \frac{I_o}{\sqrt{2}}$$

Junction transistor

It has three terminals



(a) Emitter

(b) Base


(c) Collector

Emitter is heavily doped, collector is moderately doped and base is thin and lightly doped.

Symbol

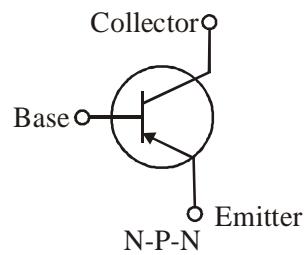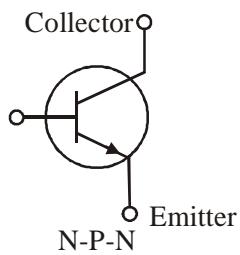

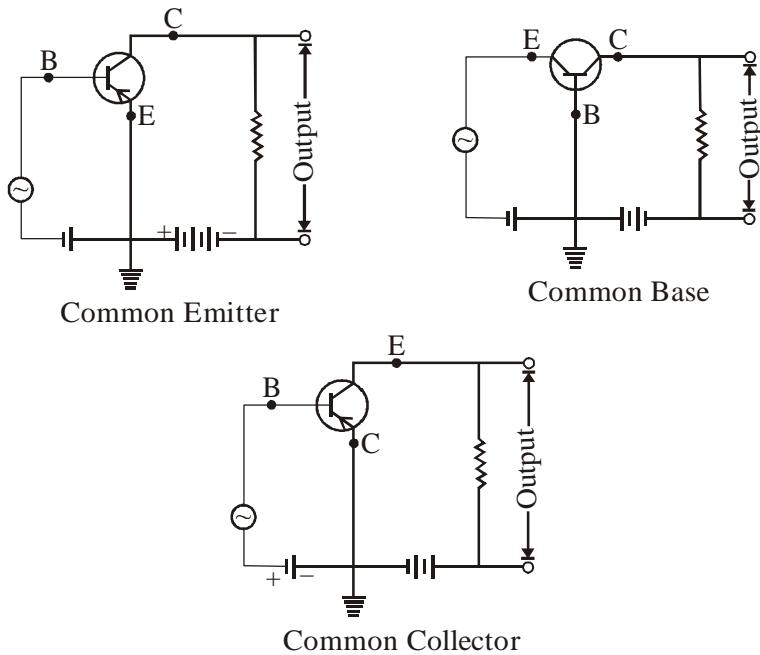A transistor can be operated in three different modes. Common-emitter, common collector and common base.



### Transistor as an Amplifier

#### 1. Common base :

In this type amplifier, base to emitter junction is forward biased whereas base to collector is reverse biased  
Transistor parameter

$$\text{Current again} = \alpha = \frac{I_0}{I_E}; \quad \text{AC current gain} = \frac{\Delta I_c}{\Delta I_e}$$

$$\text{Voltage gain} = A_v = \frac{\Delta v_o}{\Delta v_i} = \frac{I_0 R_{out}}{I_E R_{in}} = \text{Current gain} \times \text{Resistance gain} = \alpha \times \frac{R_o}{R_i}$$

Where  $R_o$  = Resistance of the output circuit

$R_i$  = Resistance of the input circuit

Power gain =  $\alpha^2 \times$  Resistance gain

#### 2. Common emitter amplifier

$$\text{Current gain} \quad \beta = \frac{\Delta I_c}{\Delta I_b}$$


$$\text{Voltage gain } (A_v) = \text{Current gain} \times \text{Resistance gain} = \beta \times A_v$$

$$\text{Power gain} = \beta^2 \times \text{Resistance gain}$$

$$\text{Resistance gain} = \frac{R_o}{R_i}$$

Transistor used as an oscillator converts D.C. into A.C.

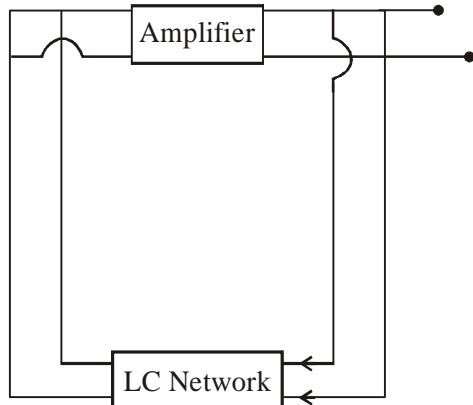Amplifier section is just a transistor used in common-emitter mode.




$$f_0 = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

Part of output energy is sent back in phase to input circuit. This is also called positive feed back.

MARKS



# MARKS

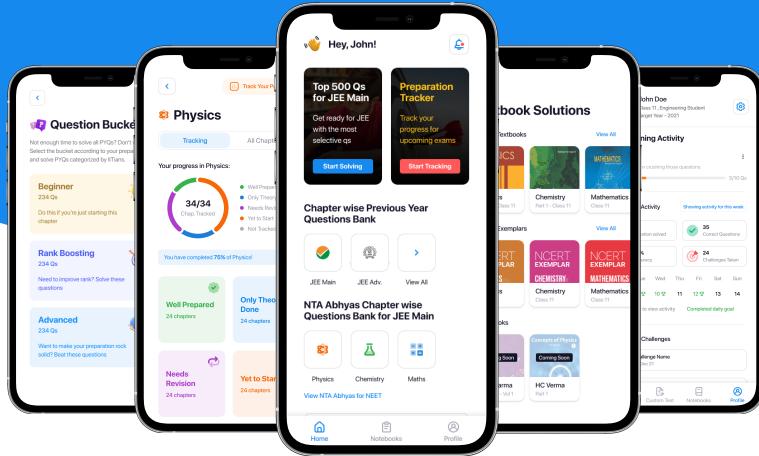

## The only app you need to prepare for



JEE MAIN



JEE ADV.



BITSAT



WBJEE



MHT CET



and more...



4.8

Rating on Google Play

50,000+

Students using daily

2,00,000+

Questions available

### With MARKS app you can do all these things for free 😍

- ✓ Solve Chapter-wise PYQ of JEE Main, JEE Advanced, NEET, BITSAT, WBJEE, MHT CET & more
- ✓ Create Unlimited Custom Tests for any exam
- ✓ Attempt Top Questions for JEE Main which can boost your rank
- ✓ Track your exam preparation with Preparation Trackers
- ✓ Complete daily goals, rank up on the leaderboard & compete with other aspirants



4.8

Rating on Google Play

50,000+

Students using daily

2,00,000+

Questions available

